


(notes revised from the resources of the textbook)

## 10.1 Simple Adders

. Half adder: 2 inputs


 $c = x \text{ AND } y$  (carry) $s = x \text{ XOR } y$  (sum)

Inputs		Outputs	
$x$	$y$	$c$	$s$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


. Full adder: 3 inputs

Inputs			Outputs	
$x$	$y$	$c_{in}$	$c_{out}$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Binary half-adder (HA) and full-adder (FA).

## Full-Adder Implementations

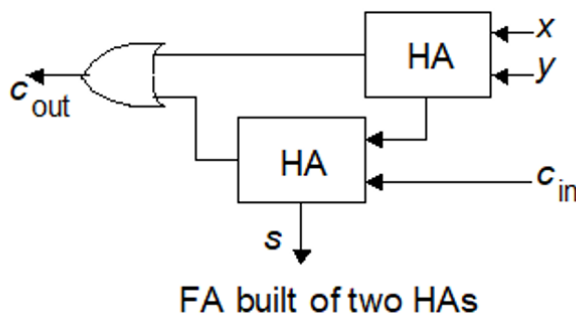

Full adder implemented with two half-adders,

## .Ripple-Carry Adder: Slow But Simple

 


Figure 10.4 Ripple-carry binary adder with 32-bit inputs and output.

## 10.2 Carry Propagation Networks

To design the fast adder, the delay of carry generations should be avoided. We introduce a carry propagation networks.

eg.  $x+y$

First, define  $g_i = x_i \cdot y_i$  (logical and),  $p_i = x_i \oplus y_i$   
 if  $g_i = 1$ , a new carry is generated

$$\begin{array}{r}
 x_i = 1, y_i = 1 \\
 \quad 1 \\
 + \quad 1 \\
 \hline
 = 10 \\
 \quad \uparrow \text{a new carry is generated}
 \end{array}$$

$$\begin{array}{r}
 x_i = 0, y_i = 1 \\
 \quad 0 \\
 + \quad 1 \\
 \hline
 = 1 \quad \text{No Carry}
 \end{array}$$

1. a new carry is generated  $\underline{g_i}=1$ , or
2. an input carry is propagated to the next bit  $p_i=1$  and  $c_i=1$


## Ripple-Carry Adder Revisited

Latency of  $k$ -bit adder is roughly  $2k$  gate delays:

3

## 10.3 Counting and Incrementation

Increase by a,  $x = x + a$

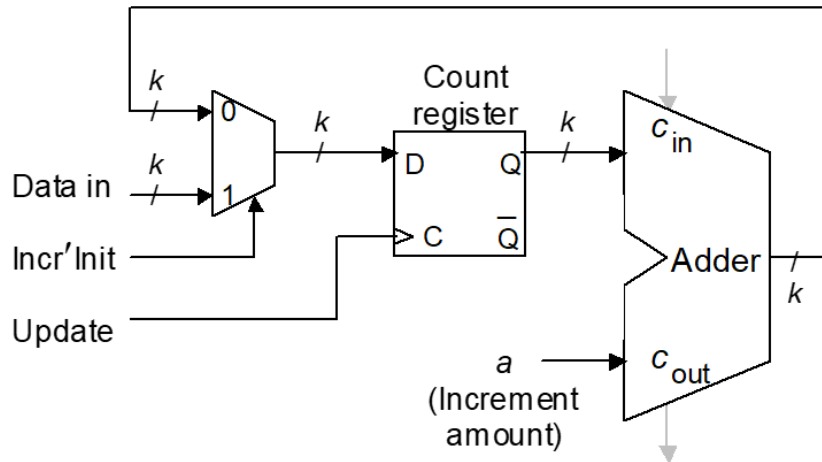

Schematic diagram of an initializable synchronous counter.

## 10.4 Design of Fast Adders

carries can be computed directly without delay

In the carry-lookahead adders, the i-th carry is obtained from the input of  $g_j, p_j, C_0$  ( $0 \leq j \leq i-1$ )

$$C_1 = G_0 + P_0 \cdot C_0,$$

$$C_2 = G_1 + P_1 \cdot C_1,$$

$$C_3 = G_2 + P_2 \cdot C_2,$$

$$C_4 = G_3 + P_3 \cdot C_3.$$

Substituting  $C_1$  into  $C_2$ , then  $C_2$  into  $C_3$ , then  $C_3$  into  $C_4$  yields the following expanded equations:

$$C_1 = G_0 + P_0 \cdot C_0,$$


$$C_2 = G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1,$$

$$C_3 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2,$$

$$C_4 = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3 + C_0 \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3.$$

When designing 32-bit fast adder, in order to make it simpler, we separate the 32-bit into 8 groups, each group has 4 bits.

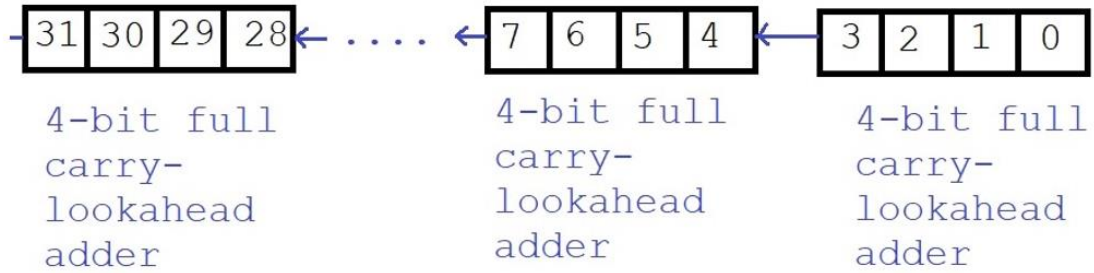
Inside each group, we use 4-bit full carry-lookahead adder. Between the groups, the structure of ripple-carry adder are applied.


 
## 10.5 Logic and Shift Operations

Logic and, or, nor, xor can be implemented by the corresponding gates.

Shifts can be implemented by multiplexing.




Multiplexer-based logical shifting unit.
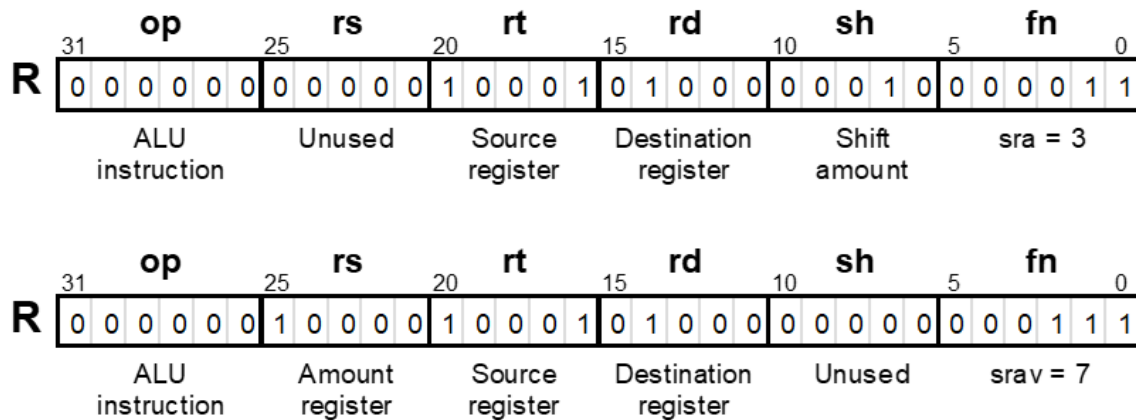
# Arithmetic Shifts


Purpose: Multiplication and division by powers of 2

```
sra $t0,$s1,2 # $t0 ← ($s1) right-shifted by 2
srav $t0,$s1,$s0 # $t0 ← ($s1) right-shifted by ($s0)
```



The two arithmetic shift instructions


## Shifting in Multiple Stages

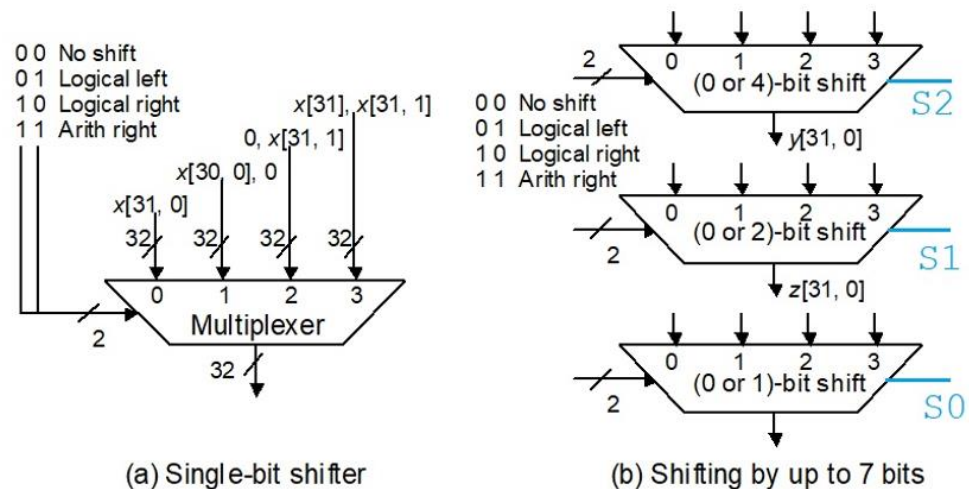


S2 S1 S0: 1 0 1	shift 5 bits	1 1 1	shift 7 bits
0 1 1	shift 3 bits	1 0 0	shift 4 bits

Multistage shifting in a barrel shifter.

## 10.6 Multifunction ALUs

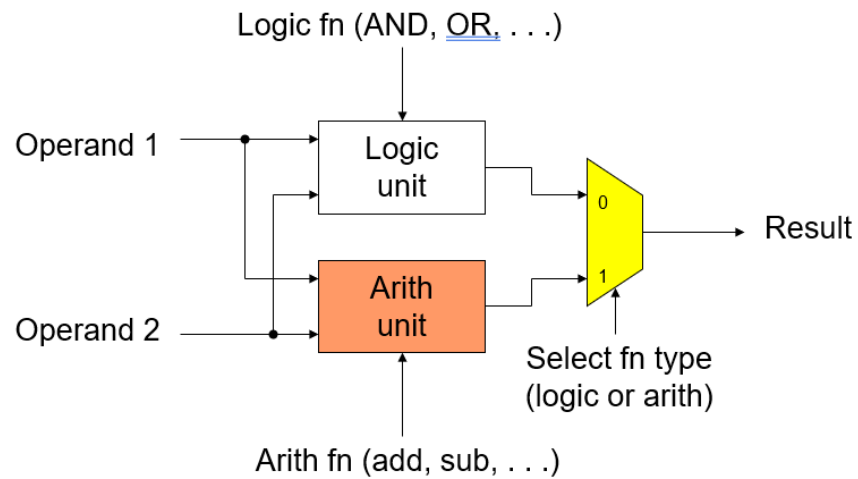

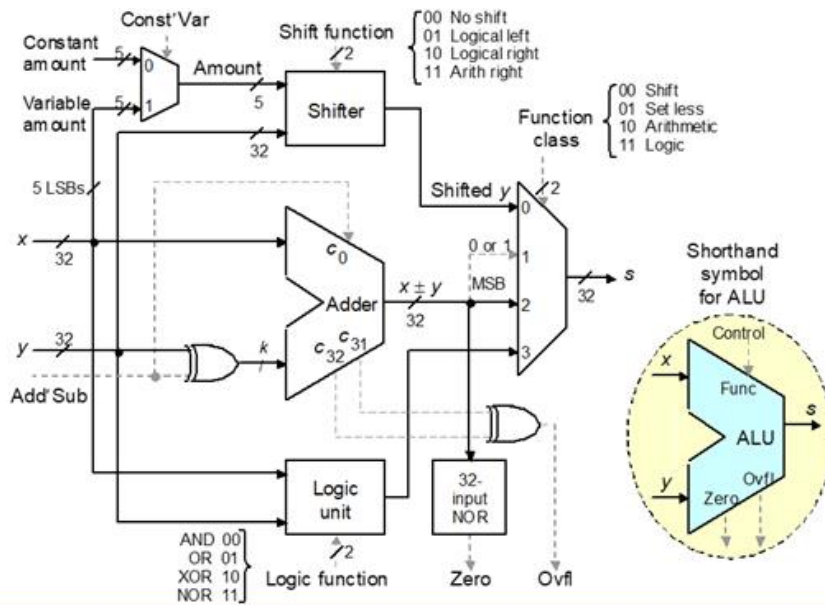General structure of a simple arithmetic/logic unit.



A multifunction ALU with 8 control signals (2 for function class, 1 arithmetic, 3 shift, 2 logic) specifying the operation.